

# Calculation Report: Monolithic Power Amplifier PRO-Q2

Daan Conijn, 13023217  
Andrew Lau, 13058339  
Kevin Oei, 13090062  
Koen van Vliet, 13093053  
Group 1

EQ2.a  
EQ2.c

April 4th, 2015

## <sup>5</sup> 1 Introduction

In this calculation report the monolithic power amplifier is determined and calculated.

## 2 Monolithic Power Amplifier

### 2.1 Requirements

10 The power amplifier has the following specifications:

- Input impedance of at least  $50\text{ k}\Omega$
- Output power:  $15\text{ W}$  sine in  $R_{\text{load}} = 8\text{ }\Omega$  at  $1\text{ kHz}$
- Frequency range:  $10\text{ Hz}$  to  $100\text{ kHz}$  ( $-3\text{ dB}$ ) at  $P_{\text{load}} = 0.5\text{ W}$  in  $8\text{ }\Omega$

### 2.2 Chosen Power Amplifier

15 For the power amplifier, the LM1875 (Farnell code: 1468913) was chosen. This specific power amplifier has been chosen because the LM1875 meets the specified requirements.

### 2.3 Calculations

20 For determining the maximum output voltage and current, it is assumed the amplifier drives an  $8\text{ }\Omega$  load at  $15\text{ W}$ .

The formula for the power equals to:

$$P = U * I \quad (1)$$

Therefore the following formulas can be derived:

$$U_{OUT,max} = \sqrt{P * R} = \sqrt{15 * 8} = 11V \quad (2)$$

$$I_{OUT,max} = \sqrt{\frac{P}{R}} = \sqrt{\frac{15}{8}} = 1,37A \quad (3)$$

25 The amplifier has a bandwidth of  $70\text{ kHz}$  at  $20\text{ W}$  output power, however the desired dynamic range of  $10\text{ Hz}$  to  $100\text{ kHz}$  can be easily achieved at lower power output.

According to the datasheet from LM1875 [1] the supply voltage need to be approximately  $\pm 18\text{ V}$  to accomodate to the  $15\text{ W}$  output power.

## References

- [1] Texas Instruments. (2004, May). “*LM1875 20W Audio Power Amplifier*”  
30 [online]. Available: <http://www.farnell.com/datasheets/1703151.pdf> [April  
3, 2015].